

1 Construct a truth table for ...

A)  $x\bar{y}z + \bar{x}yz + x\bar{y}\bar{z}$

x	y	z	$x\bar{y}z$	$\bar{x}yz$	$x\bar{y}\bar{z}$	$F(x,y,z)$
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	0	0	0
0	1	1	0	1	0	1
1	0	0	0	0	1	1
1	0	1	1	0	1	1
1	1	0	0	0	1	1
1	1	1	0	0	0	0

\* DeMorgan's:  $\bar{x}\bar{y} = \overline{x+y}$   
 $\Rightarrow x\bar{y}z + (\bar{x}+\bar{y})z + x(\bar{y}+\bar{z})$

B)  $(x+\bar{z})(y+z)(\bar{x}+\bar{y})$

x	y	z	$(x+\bar{z})$	$(y+z)$	$(\bar{x}+\bar{y})$	$F(x,y,z)$
0	0	0	1	0	1	0
0	0	1	0	1	1	0
0	1	0	1	1	1	1
0	1	1	0	1	1	0
1	0	0	1	0	1	0
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0

2

4) Using DeMorgan's Law, write an expression for the complement of F

If  $F(x,y,z) = xy + \bar{x}z + y\bar{z} \dots$

\* Replace each variable by its complement and interchange ANDs and ORs:

$\Rightarrow \bar{x}\bar{y} + x\bar{z} + \bar{y}z$

$\Rightarrow (\bar{x}+\bar{y})(x+\bar{z})(\bar{y}+z)$

\* Check w/ truth table:

x	y	z	xy	$\bar{x}\bar{z}$	$y\bar{z}$	$(\bar{x}+\bar{y})$	$(x+\bar{z})$	$(\bar{y}+z)$	$F_0$	$\bar{F}_0$
0	0	0	0	0	0	1	1	1	0	1
0	0	1	0	1	0	1	0	1	1	0
0	1	0	0	0	1	1	1	0	1	0
0	1	1	0	1	0	1	0	1	1	0
1	0	0	0	0	0	1	1	1	0	1
1	0	1	0	0	0	1	1	0	0	1
1	1	0	1	0	1	0	1	1	1	0
1	1	1	1	0	0	0	1	0	1	0

9) Show that  $x = xy + x\bar{y}$

(A) Using truth table

x	y	xy	$x\bar{y}$	$F(xy)$
0	0	0	0	0
0	1	0	0	0
1	0	0	1	1
1	1	1	0	1

(B) Using Boolean Identities

$$\begin{aligned}
 &\rightarrow \text{Start by simplify } xy + x\bar{y} \\
 &= xy + x\bar{y} \\
 &= x(y + \bar{y}) \quad [\text{Distributive}] \\
 &= x(1) \quad [\text{Inverse}] \\
 &= x \quad [\text{Identity}]
 \end{aligned}$$

11) Simplify the Boolean expression using algebraic identities. List the identity used at each step...

$$\begin{aligned}
 \textcircled{C} \quad F(x,y,z) &= \overline{(x+y)}(\bar{x}+\bar{y}) \\
 &= (\bar{x}\bar{y})(\bar{x}+\bar{y}) \quad [\text{DeMorgan's : OR}] \\
 &= (\bar{x}\bar{y})(\bar{x}\bar{\bar{y}}) \quad [\text{DeMorgan's : OR}] \\
 &= (\bar{x}\bar{y})(x+y) \quad [\text{Double complement}] \\
 &= (\bar{y}\bar{x})(xy) \quad [\text{commutative}] \\
 &= \bar{y}(\bar{x}x)y \quad [\text{Associative}] \\
 &= (\bar{y}y)(\bar{x}x) \quad [\text{commutative}] \\
 &= 0 \cdot 0 \quad [\text{Inverse}] \\
 &= 0
 \end{aligned}$$

15) Simplify the Boolean expression. List the identity used at each step ...

③  $\bar{x}(\bar{y}z + yz) + xyz$

$$\begin{aligned}
 &= \bar{x}z(\bar{y} + y) + xyz \quad [\text{distributive}] \\
 &= \bar{x}z(1) + xyz \quad [\text{inverse}] \\
 &= \bar{x}z + xyz \quad [\text{identity}] \\
 &= z(\bar{x} + xy) \quad [\text{distributive}] \\
 &= z(\bar{x} + xy) \\
 &= \bar{x}yz + \bar{x}yz + xyz \quad [\text{distributive}] \\
 &= \bar{x}yz + yz(\bar{x} + x) \quad [\text{distributive}] \\
 &= \bar{x}yz + yz(1) \quad [\text{inverse}] \\
 &= \bar{x}yz + yz \quad [\text{identity}] \\
 &= z(\bar{x}y + y) \quad [\text{distributive}] \\
 &= z(\bar{x} + y) \quad [\text{DeMorgan's}]
 \end{aligned}$$

→ Let  $F(x,y,z) = \bar{x}(\bar{y}z + yz) + xyz$ ,  $F_1(x,y,z) = z(\bar{x} + xy)$ ,  $F_2(x,y,z) = z(\bar{x} + y)$

x	y	z	xy	yz	$\bar{y}z$	xyz	$(\bar{y}z + yz)$	$(\bar{x} + xy)$	$(\bar{x} + y)$	$F_1(x,y,z)$	$F_2$
0	0	0	0	0	0	0	0	1	1	0	0
0	0	1	0	0	1	0	1	1	1	1	1
0	1	0	0	0	0	0	0	1	1	0	0
0	1	1	0	1	0	0	1	1	0	0	1
1	0	0	0	0	0	0	0	0	0	0	0
1	0	1	0	0	1	0	1	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0	0
1	1	1	1	1	0	1	1	1	1	1	1

→ Check with Karnaugh map:

- 8 minterms

x	y	z	
0	0	0	$\bar{x}\bar{y}\bar{z}$
0	0	1	$\bar{x}\bar{y}z$
0	1	0	$\bar{x}y\bar{z}$
0	1	1	$\bar{x}yz$
1	0	0	$x\bar{y}\bar{z}$
1	0	1	$x\bar{y}z$
1	1	0	$xy\bar{z}$
1	1	1	$xyz$

x	yz			
	00	01	11	10
0	0	0	1	0
1	0	0	1	0

$(\bar{x}z + yz)$

0  
1  
0  
0  
0  
1  
0  
1

Group A:  $001 + 011 \rightarrow \bar{x}yz + \bar{x}yz \Rightarrow \bar{x}z$

Group B:  $011 + 111 \rightarrow \bar{x}yz + xyz \Rightarrow yz$

⇒ Group A + Group B:  $\bar{x}z + yz$

21) Write the Boolean expression in sum-of-products form...


x	y	z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

$$\Rightarrow F(x,y,z) = \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} + x y \bar{z}$$

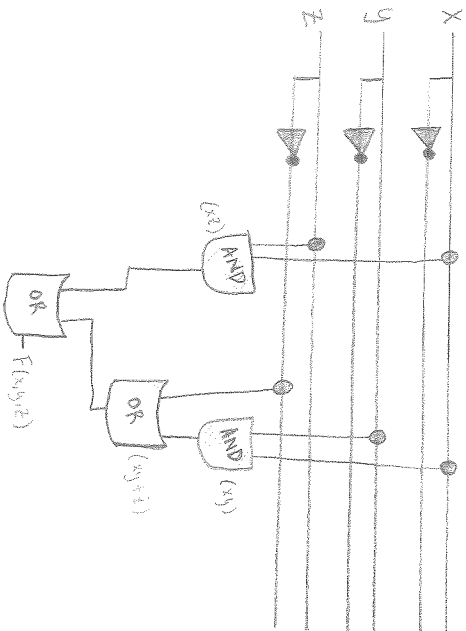
29) Draw the combinational circuit that directly implements the Boolean expression:

$$F(x,y,z) = xz + (xy + \bar{z})$$

→ For n inputs,  $2^n$  possible combinations  $\Rightarrow 2^3 = 8$  combinations



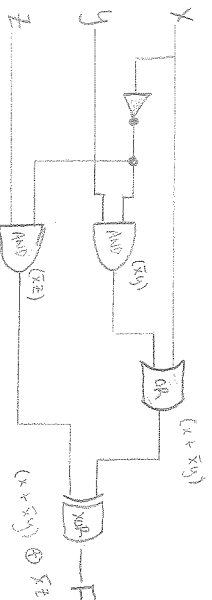
32) Find the truth table that describes the circuit:



x	y	$\overline{xy}$	F
0	0	1	0
0	1	0	1
1	0	1	1
1	1	0	0

x	y	z	$\bar{x}y$	$\bar{x}\bar{z}$	$(x + \bar{x}y)$	F
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	1	0	1	1
0	1	1	1	0	1	0
1	0	0	0	1	1	1
1	0	1	0	0	1	1
1	1	0	0	0	1	1
1	1	1	0	0	1	1

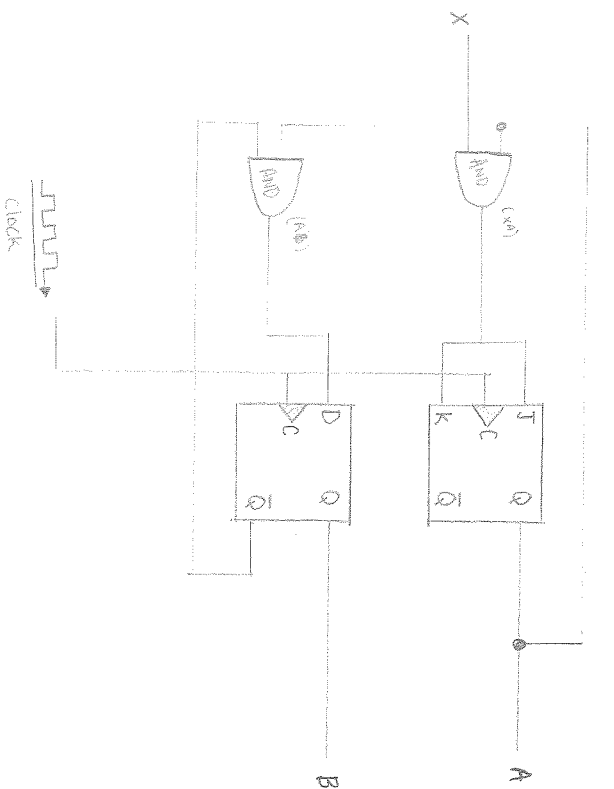
50) Complete the truth table for the sequential circuit :



NEXT STATE			
A	B	X	B
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

59) Construct a Moore machine that counts modulo 5 :

→ 5 possible outcomes : 0, 1, 2, 3, 4

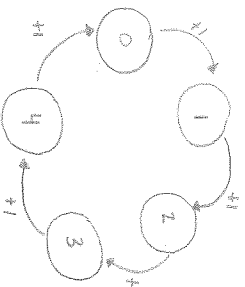

$$\left\{ \begin{array}{l} 0 \bmod 5 = 0 \\ 1 \bmod 5 = 1 \\ 2 \bmod 5 = 2 \\ 3 \bmod 5 = 3 \\ 4 \bmod 5 = 4 \end{array} \right.$$

Note  
5 mod 5 = 0  
6 mod 5 = 1  
...

3

2a) Create the K-maps and then simplify the function :

$$F(x, y, z) = \bar{x}\bar{y}\bar{z} + \bar{x}yz + \bar{x}y\bar{z}$$

x	yz			
	00	01	11	10
0	1	0	1	0
1	0	0	0	1

$$\Rightarrow A+B = \bar{x}y + \bar{x}\bar{z} \quad [\text{distributive}]$$


$$= \bar{x}(y + \bar{z})$$

$$\text{Group A: } 011 + 010 \Rightarrow \bar{x}y\bar{z} + \bar{x}y\bar{z}$$

$$\Rightarrow \bar{x}y$$

$$\text{Group B: } 000 + 010 \Rightarrow \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} \Rightarrow \bar{x}\bar{z}$$

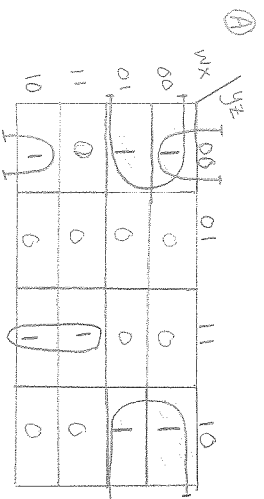3) Write a simplified expression for the Boolean function defined by the following Karnaugh Maps...




$$\text{Group A: } 0000 + 0100 + 0010 + 0110 \Rightarrow \bar{w}\bar{x}\bar{y}\bar{z} + \bar{w}x\bar{y}\bar{z} + \bar{w}\bar{x}y\bar{z} + \bar{w}x y\bar{z}$$

$$+ \bar{w}x y \bar{z} \Rightarrow \bar{w}\bar{z}$$

$$\text{Group B: } 0000 + 1000 \Rightarrow \bar{w}\bar{x}\bar{y}\bar{z} + w\bar{x}\bar{y}\bar{z} \Rightarrow \bar{x}\bar{y}\bar{z}$$

$$\text{Group C: } 1111 + 1011 \Rightarrow wxy\bar{z} + w\bar{x}y\bar{z} \Rightarrow wy\bar{z}$$
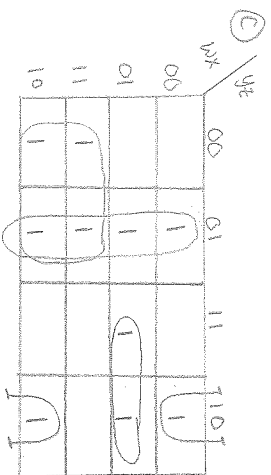
$$F(w,x,y,z) = \bar{w}\bar{z} + \bar{x}\bar{y}\bar{z} + wy\bar{z}$$



$$\text{Group A: } 1100 + 1000 + 1101 + 1001 \Rightarrow w\bar{y}$$

$$\text{Group B: } 0001 + 0101 + 1101 + 1001 \Rightarrow \bar{y}z$$

$$\text{Group C: } 0111 + 0110 \Rightarrow \bar{w}xy$$

$$\text{Group D: } 0010 + 1010 \Rightarrow \bar{x}y\bar{z}$$

$$F(w,x,y,z) = w\bar{y} + \bar{y}z + \bar{w}xy + \bar{x}y\bar{z}$$