

**Homework #4**  
**Due April 11, 2015**  
**CIS 4930/6930: Low Power VLSI Design**

**Notes:**

- 1. The homework will be done and the report must be submitted individually.**
- 2. Submit schematics, measurement files, netlist, plot of signals to get full credit**


Q1. Input vector control for leakage power reduction: This exercise will focus on input conditioning for low power. Assume two stacked NMOS transistors of size  $1\mu/0.03\mu$  each and  $V_{dd}=1V$  as shown below. For the simulations assume temperature=110C

- (a) Find input conditions A and B that minimizes the subthreshold leakage.
- (b) Find input conditions A and B that minimizes the gate leakage.
- (c) Find input conditions A and B that minimizes the junction leakage.

To get full credit in above questions plot leakages for all four combinations of A and B (00,01,10,11). Any plotting software (excel, matlab, gnuplot) can be used.

- (d) Fix  $A=0$  and  $B=0$ . Next sweep the channel length of both transistors from 30nm to 180nm in steps of 10nm and plot subthreshold leakage vs channel length. Explain the observation.

(10+10+10+20)

 

Q2. Read the paper “low power CMOS digital design” posted in canvas and answer following questions:

- (a) Between static and dynamic logic, which one is good for low power and why? (Be specific but don't write thesis).
- (b) For low power should we increase the transistor sizing or reduce it? Explain the tradeoff.
- (c) How logic duplication helps in lowering the power consumption? Explain with power equation and example.
- (d) How pipelining helps in lowering the power consumption? Explain with power equation and example.
- (e) Is it possible to continue logic duplication infinitely to keep lowering voltage and reduce power? If not, what sets the limits for logic duplication?

(10+10+10+10+10)