

CDA 3201 Homework 4

Chapter 7: Finite State Machines

Due to: Tuesday 07/15/2014

Turn in as hardcopy format in class

10 bonus points for typed homework

1) (10 pts) Design a 4-bit mod-10 up-counter that counts in the following sequence:

0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001, 0000...(wraps around)


- Draw the **Moore** state diagram and next-state table
- Implement the counter using T flip-flops (derive the simplified next-state equations)
- Is this a self-starting counter or a non-self-starting counter? Justify your answer.
- Draw another state diagram for this circuit which starts in the *unused* state 1011.

2) (10 pts) Implement a base 13 up-counter using 74163

3) (10 pts) Implement a base 26 up-counter using only one 74163

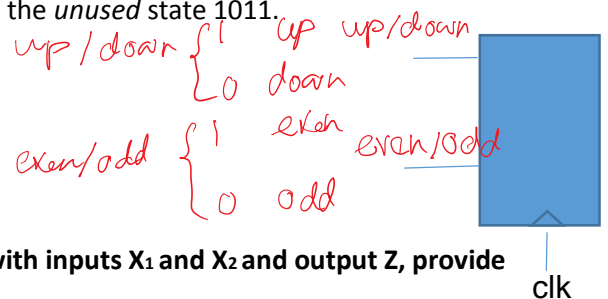4) (20 pts) Implement a 5-bit up/down, even/odd counter

odd sequence: 1, 3, 5, 7, ...
even sequence: 0, 2, 4, 6, 8, ...



5) (10 pts) Given the following specifications of a **Moore** machine with inputs X_1 and X_2 and output Z , provide the state diagram:

- The input sequence $X_1X_2 == 01, 11$ causes the output z to become 0
- The input sequence $X_1X_2 == 10, 11$ causes the output z to become 1
- The input sequence $X_1X_2 == 10, 01$ causes the output z to toggle

6) (10 pts) Given the following specifications of a sequential circuit with one input X and one output Z , provide the **Mealy** state diagram for each of the following cases (3 diagrams total):

- Output z toggles if the total number of ones is odd.
- Output $z = 1$ if and only if the total number of 1's is divisible by 2 (ex: 0, 2, 4 ...)
- Output $z = 1$ if the total number of 0's is divisible by 3 (ex: 0, 3, 6 ...)

7) (10 pts) A finite state machine has one input and one output. The output becomes 1 and remains one after at least three logic '0's and at least one logic '1' has occurred as input. Order does not matter. Implement this as a **Moore** machine. Provide the following:

- Moore state diagram
- State transition table

8) (20 pts) Design a controller for a newspaper vending machine to the following specification. The newspaper costs 25 cents. The vending machine accepts nickels, dimes, and quarters. The customer will press a START button and begin inserting coins (assume after each coin is inserted, your FSM will move to the next state). If exact change is entered, a control signal (**UNLATCH**) is asserted and the machine is unlocked - the customer can take a newspaper. After this, a control signal (**REL**) will be asserted indicating the money should be deposited in the main repository. If the customer overpays for the paper, the deposited coins are refunded to the customer by asserting a (**REF**) signal (assume once the coins are inserted, they are held in a separate location and do not have to be released individually). Provide the following:

- Mealy** state diagram
- State transition table